

EPROM MUSIC

By Sebastian Tomczak
Electronic Music Unit, Elder Conservatorium of Music, University of Adelaide

CONCEPT

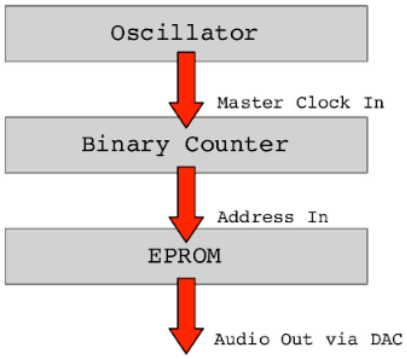The idea behind EPROM MUSIC is to explore digital sound and music that does not require any programmable parts of any variety. An oscillator is connected to a binary counter, which in turns clocks out samples stored in an EPROM chip. A DAC circuit provides an audio output.



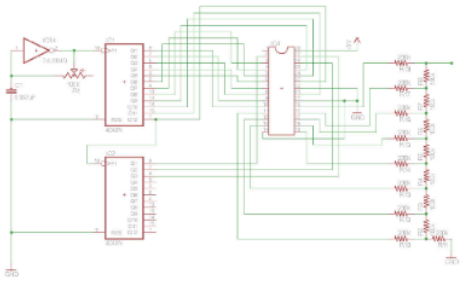



SAMPLE LOOP PLAYBACK

A short loop can be loaded onto the EPROM , and played back at a speed / pitch determined by the frequency of the initial oscillator. By manipulating the address inputs of the EPROM, sections of the loop can be isolated and stuttering and glitching can be achieved easily.

DRUM MACHINE

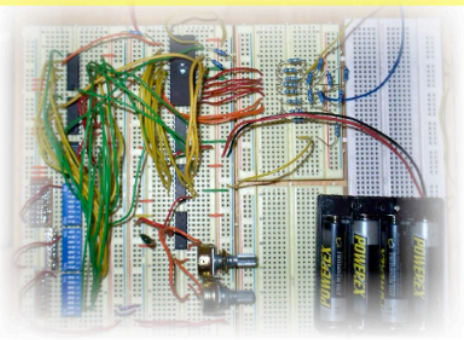Multiple drum samples can be loaded onto the EPROM, and then a series of buttons or switches can trigger the address range corresponding to each individual sound. Thus, a simple logic-based drum machine can be constructed. The highest address bit can toggle between two separate drum kits.



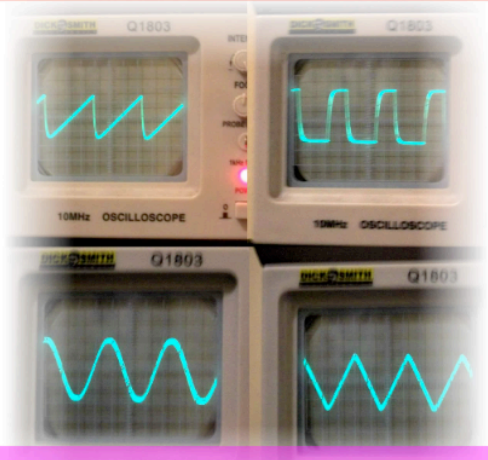

WAVEFORM SYNTHESIS

A set of many waveforms can be loaded onto the EPROM. The waveforms are shaped and formatted using a Max/MSP patch, specially designed for the task. Each waveform contains 128 samples. The higher address bits are then used to select between waveforms. By manipulating the address bits, grain and glitch-like artefacts can be introduced into the audio output.

EXTENSION

This concept can be extended easily. The system is modular, in that multiple EPROMs can run from the same clock. Different grooves and triplets can be achieved by adding a decade counter, for instance.

Schematics, patches etc: http://little-scale.blogspot.com/search/label/eprom%20music